



**VIVEKANAND EDUCATION SOCIETY'S INSTITUTE OF  
TECHNOLOGY**  
CHEMBUR, MUMBAI 400074

**DESIGN WITH LINEAR INTEGRATED CIRCUITS  
(ELX 504)**

**COURSE PROJECT**  
**“ARDUINO CONTROLLED VARIABLE GAIN AMPLIFIER”**

**SUBMITTED BY**

<b>STUDENT NAME</b>	<b>ROLL NUMBER</b>
REETI KOTHARI	28
ATIQUE KUDCHI	29
AARYAA PADHYEGURJAR	40
GIRISH PAWAR	46

OF  
TE – (D11A)

**DEPARTMENT OF ELECTRONICS ENGINEERING**  
**UNDER THE GUIDANCE OF**  
**Mr YOGESH PANDIT**



**VIVEKANAND EDUCATION SOCIETY'S INSTITUTE OF  
TECHNOLOGY**

CHEMBUR, MUMBAI 400074

**CERTIFICATE OF APPROVAL OF COURSE PROJECT**

THIS IS TO CERTIFY THAT

**REETI KOTHARI, ATIQUE KUDCHI, AARYAA PADHYEGURJAR AND GIRISH PAWAR** OF THIRD YEAR "ELECTRONICS ENGINEERING" STUDYING UNDER THE UNIVERSITY OF MUMBAI HAVE SATISFACTORILY PRESENTED THE PROJECT ON **"ARDUINO CONTROLLED VARIABLE GAIN AMPLIFIER"** AS A PART OF THE COURSE WORK OF COURSE PROJECT FOR SEMESTER V IN THE ACADEMIC YEAR 2018-19.

DATE:

INTERNAL EXAMINER

# Index


<b>Sr No</b>	<b>Title</b>	<b>Page Number</b>
1	Introduction	3
2	Block Diagram	3
3	Circuit Diagram	4
4	Components	5
5	Working	6
6	PCB Layout	8
7	Observation Table	9
8	Calculation	10
9	Advantages	11
10	Disadvantages	11
11	Applications	11
12	Conclusion	12
13	References	12

## I. Introduction


There are many instances when a variable gain op-amp circuit may be required. Although it is possible to place a potentiometer on the output of a circuit, there are more elegant ways in which this can be achieved, maintaining levels of impedance more accurately. Such a circuit is the Variable Gain Amplifier (VGA).

Variable gain amplifiers (VGAs) are signal-conditioning amplifiers with electronically settable voltage gain. A simple VGA consists of a few resistors with different values, a network of resistors, an operational amplifier and components that switch between these resistors. In our project, we have used a CMOS Quad Bilateral Switch (CD4016BE) to perform this function. It has 4 switches with individual controls, which are controlled using the Arduino board.

## II. Block Diagram

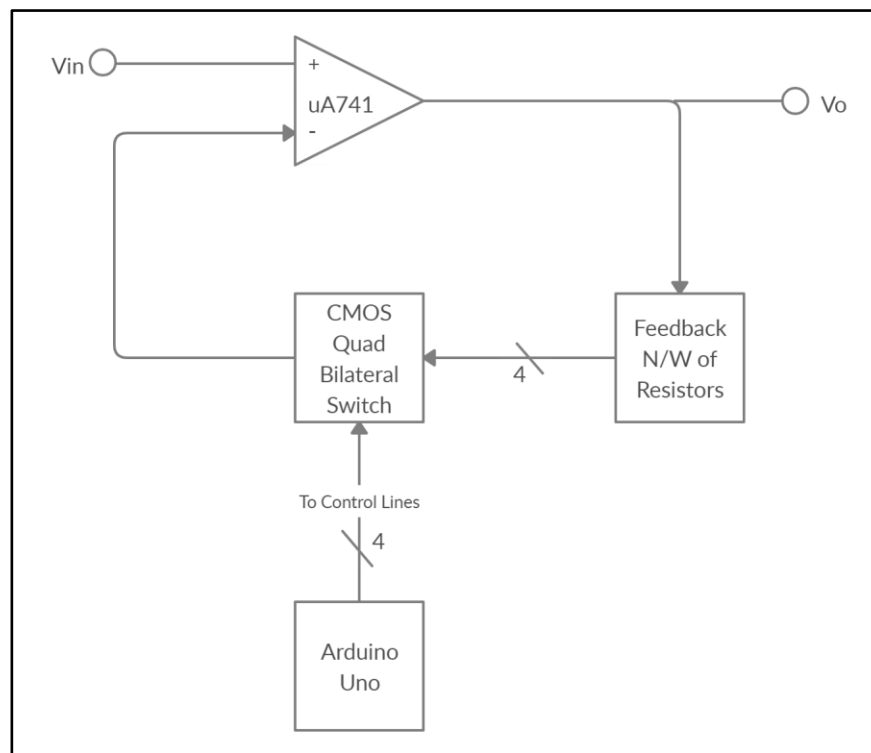

### III. Circuit Diagram

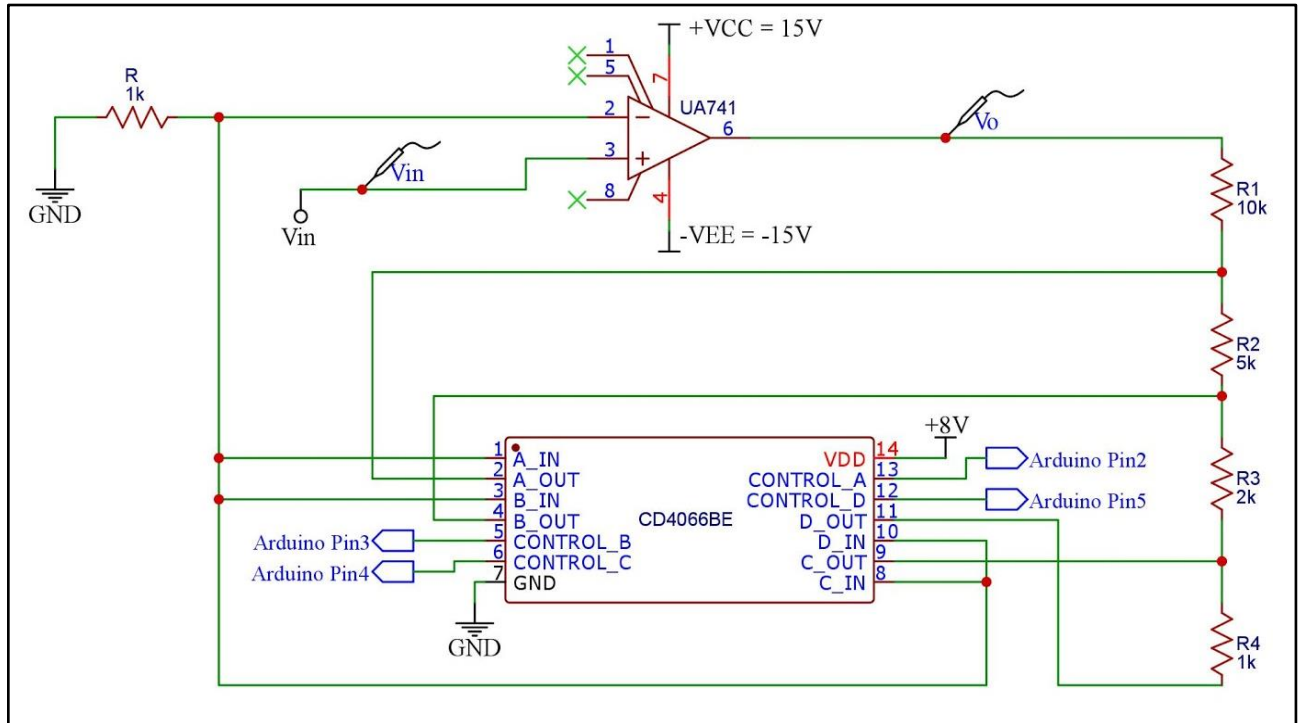

## IV. Components

Sr. no	Name	Values/ Number	Quantity
1	Op-Amp IC	uA 741 ( $\pm 15V$ )	1
2	CMOS Quad Bilateral Switch IC	CD4016BE (Max +10V input)	1
3	Microcontroller	Arduino Uno & IDE	1
4	Resistors	1 k $\Omega$ 2k $\Omega$ 5 k $\Omega$ 10 k $\Omega$	2 1 1 1

## V. Working

1. The circuit works on the simple principle of changing the feedback resistor values to vary the gain accordingly.
2. The digital pins 2,3,4,5 from the Arduino are set to output mode, subsequently giving a digital output of 5V (HIGH) and 0V (LOW) whenever specified by the code.
3. These outputs are connected to feedback resistors in the circuit.
4. Whenever we input any number from 0 to 9 into the software, the 4 pins represent a binary number. For Example, if we input number 5 as a command on the Arduino Serial Monitor, the output of the Arduino will be (2,3,4,5) = (1010).
5. The pins which are HIGH (1) will provide an active high control signal to the control pins of the respective switches of CD4016BE Switch IC. Each of these switches is connected to the resistor feedback network, thus giving us a different feedback value for each input.
6. We can thus easily change the gain value to a desirable point with only 2 key presses.

### Arduino Code:


```
void setup() {
  pinMode(2, OUTPUT); // to pin 13
  pinMode(3, OUTPUT); // to pin 5
  pinMode(4, OUTPUT); // to pin 6
  pinMode(5, OUTPUT); // to pin 12
  Serial.begin(9600);
}
char cmd;
void loop() {
  while (Serial.available() > 0) {
    cmd = char(Serial.read());
    if (cmd == '0') {
      digitalWrite(2, 1);
      digitalWrite(3, 0);
      digitalWrite(4, 0);
      digitalWrite(5, 0);
    }
    if (cmd == '1') {
      digitalWrite(2, 0);
      digitalWrite(3, 1);
      digitalWrite(4, 0);
      digitalWrite(5, 0);
    }
    if (cmd == '2') {
      digitalWrite(2, 0);
      digitalWrite(3, 0);
      digitalWrite(4, 1);
      digitalWrite(5, 0);
    }
    if (cmd == '3') {
      digitalWrite(2, 0);
      digitalWrite(3, 0);
      digitalWrite(4, 0);
      digitalWrite(5, 1);
    }
  }
}
```

```
if (cmd == '4') {
    digitalWrite(2, 1);
    digitalWrite(3, 0);
    digitalWrite(4, 0);
    digitalWrite(5, 1);
}
if (cmd == '5') {
    digitalWrite(2, 1);
    digitalWrite(3, 0);
    digitalWrite(4, 1);
    digitalWrite(5, 0);
}
if (cmd == '6') {
    digitalWrite(2, 1);
    digitalWrite(3, 1);
    digitalWrite(4, 0);
    digitalWrite(5, 0);
}
```

```
if (cmd == '7') {
    digitalWrite(2, 0);
    digitalWrite(3, 1);
    digitalWrite(4, 0);
    digitalWrite(5, 1);
}
if (cmd == '8') {
    digitalWrite(2, 0);
    digitalWrite(3, 1);
    digitalWrite(4, 1);
    digitalWrite(5, 0);
}
if (cmd == '9') {
    digitalWrite(2, 0);
    digitalWrite(3, 0);
    digitalWrite(4, 1);
    digitalWrite(5, 1);
}
}
}
```



## VI. PCB Layout

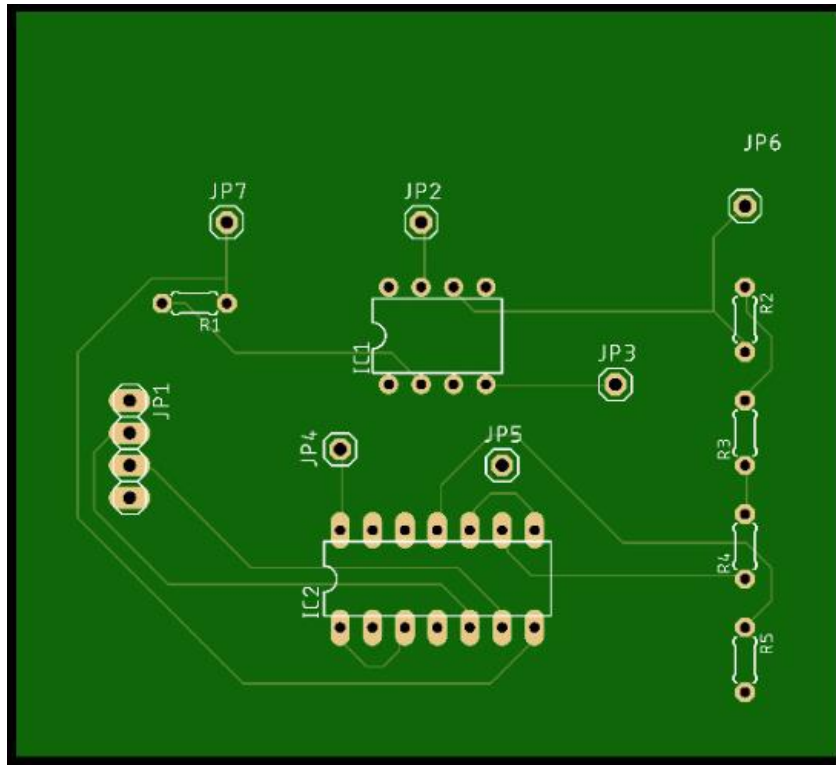

## VII. Observation Table

Practical								Theoretical	
Command on Serial Monitor of Arduino IDE	Switch Position				Vin (mV)	Vo (V)	Gain = Vo/Vin	Rf (k $\Omega$ )	Gain = $1+R_f/R$ (R = 1 k $\Omega$ )
	A	B	C	D					
0	1	0	0	0	16	0.16	10	10	11
1	0	1	0	0	16	0.22	13.75	15	16
2	0	0	1	0	16	0.25	15.625	17	18
3	0	0	0	1	16	0.27	17.5	18	19
4	1	0	0	1	16	0.16	10	10	11
5	1	0	1	0	16	0.16	10	10	11
6	1	1	0	0	16	0.16	10	10	11
7	0	1	0	1	16	0.25	15.625	15	16
8	0	1	1	0	16	0.24	15	15	16
9	0	0	1	1	16	0.29	18.125	17	18


## VIII. Calculation

Consider cmd = 9

This corresponds to (0011) Switch Control

Hence, switches A and B are OPEN and switches C and D are CLOSED.

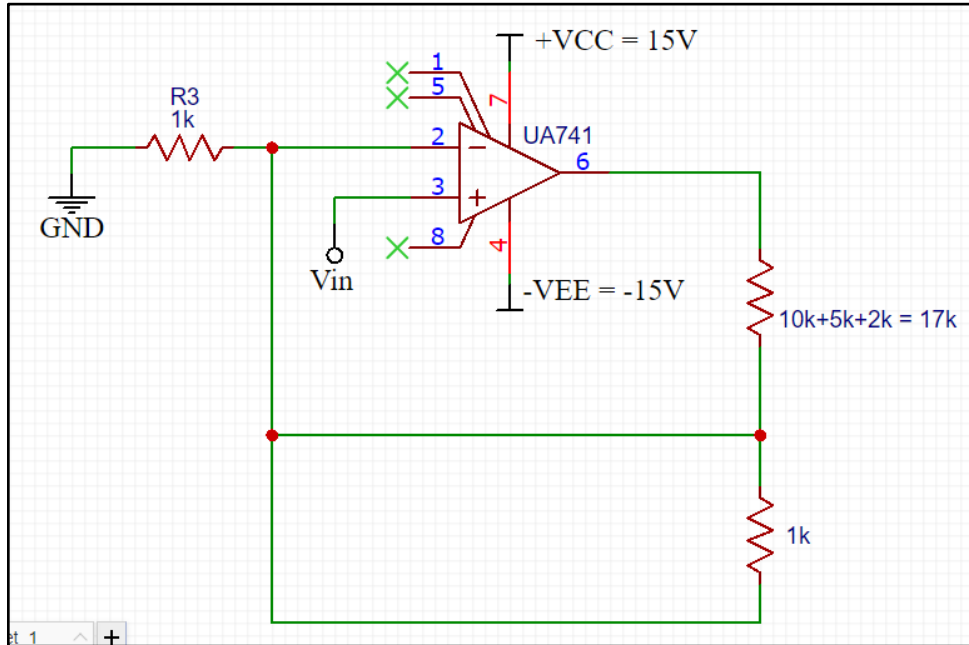According to the switch positions, the resultant circuit for this command is as follows:




Here, 1 k $\Omega$  resistor becomes redundant, and the feedback resistor is given by

$$R_f = 10 \text{ k}\Omega + 5 \text{ k}\Omega + 2 \text{ k}\Omega = 17 \text{ k}\Omega$$

Theoretical Gain =  $1 + R_f/R_1$ , Where  $R_1 = 1 \text{ k}\Omega$

$$= 1 + 17/1$$

$$= 18$$

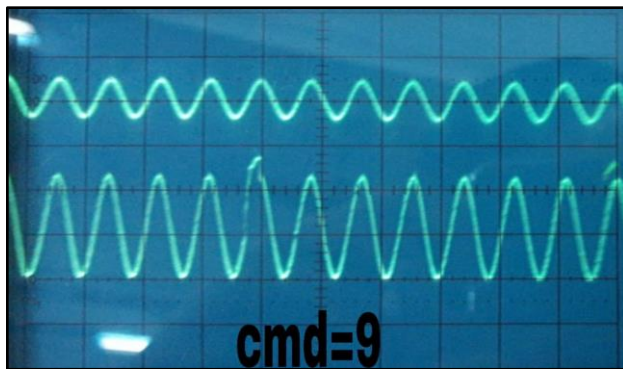

Practical Gain (Observed on CRO) = 18.125

## IX. Advantages

1. Fast switching operation
2. Non-fluctuating gain values
3. Simple circuit with high-level applications
4. Cheap and easy to manufacture and code
5. Highly accessible components
6. Changing fixed gain values is easy

## X. Disadvantages

1. Limited gain values
2. The circuit becomes bigger if more resistors are to be added
3. No option to gradually change between resistors values

## XI. Applications

1. Speech analysis
2. Radar
3. Music Industry
4. LIDAR

## XII. Conclusion

Analogue devices voltage-controlled variable gain amplifiers provide continuous gain control over a wide dynamic range for a variety of audio and optical frequency bands. VGAs improve the dynamic range of a circuit by allowing users to adjust a signal's amplitude in real-time, which is invaluable for ultrasound, speech analysis, radar, wireless communications, and instrumentation-related applications. The resulting model is a simple combination of resistors forming a feedback network whose switching action is being controlled by CMOS Quad Bilateral Switch IC CD4016BE, which in turn, can be easily manipulated by a microcontroller like the Arduino.

## XIII. References

1. [https://www.hackster.io/lucian\\_vdo/arduino-variable-gain-amplifier-c36934](https://www.hackster.io/lucian_vdo/arduino-variable-gain-amplifier-c36934)
2. <https://www.electronicdesign.com/analog/variable-gain-amplifiers>
3. Datasheet: <https://www.ti.com/lit/ds/symlink/cd4066b.pdf>
4. <https://pdfs.semanticscholar.org/29d4/a1b85673a162486749ef7a5ec06b7a6628d1.pdf>